

MAZARITA_TEAM

Alaa_Salah

Mohanad_Mohamed

Contents

1) Design Code:	2
2) Snippets:.....	11
3) Synthesis :	18
4) XDC :	20
5) Sources Files:.....	25

1) Design Code:

→ALSU:

```
module ALSU_(
    input wire [2:0] A,
    input wire [2:0] B,
    input wire [2:0] opcode,
    input wire cin,
    input wire serial_in,
    input wire direction,
    input wire red_op_A,
    input wire red_op_B,
    input wire byPass_A,
    input wire byPass_B,
    input wire clk,
    input wire rst,

    output reg valid,
    output reg [5:0] out,
    output reg [15:0] leds
);
//parameters
parameter INPUT_PRIORITY = "A";
parameter FULL_ADDER = "ON";
//internal signals
wire [15:0] led_blink;

always @(posedge clk or posedge rst) begin
    //valid <=1;
    if (rst) begin
        // reset
        out <= 'b0;
        leds <= 'b0;
        valid <= 1;
    end
    else if(byPass_A && ~byPass_B) begin
        out <= A;
        valid <= 1;
    end
    else if(byPass_B && ~byPass_A) begin
        out <= B;
    end
end
```

```

        valid <= 1;
    end
    else if(byPass_A && byPass_B) begin
        out <= INPUT_PRIORITY;
        valid <= 1;
    end
    else begin

        case (opcode)
            3'b000 : begin
                valid <= 1;                // AND
                if(red_op_A && ~red_op_B)
                    out <= &A;
                else if(~red_op_A && red_op_B)
                    out <= &B;
                else if(red_op_A && red_op_B)
                    out <= &INPUT_PRIORITY;
                else
                    out <= A & B;
            end

            3'b001 : begin
                valid <= 1;                // XOR
                if(red_op_A && ~red_op_B)
                    out <= ^A;
                else if(~red_op_A && red_op_B)
                    out <= ^B;
                else if(red_op_A && red_op_B)
                    out <= ^INPUT_PRIORITY;
                else
                    out <= A ^ B;
            end

            3'b010 : begin                // Addition
                if(red_op_A || red_op_B) begin
                    out <= 0;
                    leds <= led_blink;
                    valid <= 0;
                end
                else begin
                    valid <= 1;
                    if(FULL_ADDER == "ON")
                        out <= A + B + cin;
                    else
                        out <= A + B;
                    end
                end
            end
        endcase
    end
end

```

```

        end
    end
    3'b011 : begin                                // Multiplication
        if(red_op_A || red_op_B) begin
            out <= 0;
            leds <= led_blink;
            valid <=0;
        end
        else
            valid <= 1;
            out <= A * B;
        end
    end
    3'b100 : begin                                // Shift output
        if(red_op_A || red_op_B) begin
            out <= 0;
            leds <= led_blink;
            valid <=0;
        end
        else begin
            valid <= 1;
            if(direction)
                out <= {out[4:0], serial_in};
            else
                out <= {serial_in, out[5:1]};
            end
        end
    end
    3'b101 : begin                                // Rotation
        if(red_op_A || red_op_B) begin
            out <= 0;
            leds <= led_blink;
            valid <=0;
        end
        else begin
            valid <= 1;
            if(direction)
                out <= {out[4:0], out[5]};
            else
                out <= {out[0], out[5:1]};
            end
        end
    end
    3'b110 || 3'b111 : begin                    // Invalid opcode
        out <= 0;
        leds <= led_blink;
        valid <=0;
    end
end

```

```

        default : begin                                // to be continued
            out <= 0;
            leds <= 0;
            valid <= 1;
            end
        endcase
    end
end
blinking blink(clk,led_blink);
endmodule

```

→Blinking :

```

module blinking(clk,led );//input reset,
input wire clk;
reg [27:0] counter;
output reg [15:0] led;
reg clkout;

initial begin
    counter = 0;
    clkout = 0;
    led = 0;
end
always @(posedge clk) begin
    if (counter == 0) begin
        counter <= 149999999;//actual value used to be shown on board blinking
        //counter <= 10; to be shown in simulation
        clkout <= ~clkout;
    end else begin
        counter <= counter - 1;
    end
end

always @(posedge clkout) begin
    led <= ~led;
end
endmodule

```

→Seven_Segment Display

```

module ALSU_Display(
    input clock_100Mhz, // 100 Mhz clock source on Basys 3 FPGA
    input reset,
    input valid,
    input wire[5:0] out_ALU,
    output reg [3:0] Anode_Activate,
    output reg [6:0] LED_out
);

    reg [3:0] LED_BCD;
    reg [19:0] refresh_counter; // 20-bit for creating 10.5ms refresh period or
380Hz refresh rate
    //reg [3:0] refresh_counter; // the first 2 MSB bits for creating 4 LED-
activating signals with 2.6ms digit period
    wire [1:0] LED_activating_counter;
    //output reg [3:0] Anode_Activate, // anode signals of the 7-segment LED
display
    //output reg [6:0] LED_out// cathode patterns of the 7-segment LED display
    //=====
    always @(posedge clock_100Mhz or posedge reset)
    begin
        if(reset==1)
            refresh_counter <= 0;
        else
            refresh_counter <= refresh_counter + 1;
    end
    assign LED_activating_counter = refresh_counter[19:18];
    // anode activating signals for 4 LEDs, digit period of 2.6ms
    // decoder to generate anode signals
    always @(*)
    begin
        case(LED_activating_counter) //anode active high so invert all bits
        2'b00: begin
            Anode_Activate = 4'b1110;
            // activate LED4 and Deactivate LED2, LED3, LED1
            if(~valid)
                LED_BCD = 4'b1011;
            else LED_BCD = out_ALU[3:0];
            end
        2'b01: begin
            Anode_Activate = 4'b1101;
            // activate LED3 and Deactivate LED1, LED2, LED4
            if(~valid)
                LED_BCD = 4'b0000;
            else LED_BCD = out_ALU[5:4];
        end
    end
endmodule

```

```

        end
    2'b10: begin
        Anode_Activate = 4'b1011;
        // activate LED2 and Deactivate LED3, LED1, LED4
        if(~valid)
            LED_BCD = 4'b0100;
        else LED_BCD = 4'bxxxx;
        end
    2'b11: begin
        Anode_Activate = 4'b0111;
        // activate LED1 and Deactivate LED2, LED3, LED4
        if(~valid)
            LED_BCD = 4'b1110;
        else LED_BCD = 4'bxxxx;
        end
    endcase
end
// Cathode patterns of the 7-segment LED display
always @(*)
begin
    case(LED_BCD) // cathode active low
    4'b0000: LED_out = 7'b0000001; // "0"
    4'b0001: LED_out = 7'b1001111; // "1"
    4'b0010: LED_out = 7'b0010010; // "2"
    4'b0011: LED_out = 7'b0000110; // "3"
    4'b0100: LED_out = 7'b1001100; // "4"
    4'b0101: LED_out = 7'b0100100; // "5"
    4'b0110: LED_out = 7'b0100000; // "6"
    4'b0111: LED_out = 7'b0001111; // "7"
    4'b1000: LED_out = 7'b0000000; // "8"
    4'b1001: LED_out = 7'b0000100; // "9"

    4'b1010: LED_out = 7'b0001000; // "10--> A"
    4'b1011: LED_out = 7'b1100000; // "11--> b"
    4'b1100: LED_out = 7'b0110001; // "12--> C"
    4'b1101: LED_out = 7'b1000010; // "13--> d"
    4'b1110: LED_out = 7'b0110000; // "14--> E"
    4'b1111: LED_out = 7'b0111000; // "15--> F"
    default: LED_out = 7'b1111110; // "- activate common G only"
    endcase
end
endmodule

```

→D f/f

```
module D_Asynch(d,clk,rst,q);
input wire rst,clk;
input wire [2:0] d;
output reg [2:0] q;
//output wire [2:0] qbar;

always @(posedge clk or posedge rst) begin
    if (rst)
        q<=0;
    else begin
        q <= d;
    end
end
//assign qbar = ~q;
endmodule
```

→TopModule

```
module ALSU_TO_SEVEN_SEGMENT(
    input wire [2:0] A,
    input wire [2:0] B,
    input wire [2:0] opcode,
    input wire cin,
    input wire serial_in,
    input wire direction,
    input wire red_op_A,
    input wire red_op_B,
    input wire byPass_A,
    input wire byPass_B,
    input wire clk,
    input wire rst,

    output wire[3:0] anode,
    output wire[6:0] cathode,
    output wire[15:0] leds
);
//internal wires
wire [5:0] out_ALSU;
wire valid;
```



```

wire [2:0] A_registered,B_registered;
D_Asynch A_(A,clk,rst,A_registered);
D_Asynch B_(B,clk,rst,B_registered);
// instance for ALSU block
ALSU_
ALSU(A_registered,B_registered,opcode,cin,serial_in,direction,red_op_A,red_op_B,byPass_A,byPass_B,clk,rst,valid,out_ALSU,leds);

//instance for 7 segment display
ALSU_Display ALSU_display_on_7segment(clk,rst,valid,out_ALSU,anode,cathode);

endmodule

```

→ Test Bench

```

module ALSU_TO_SEVEN_SEGMENT_tb();
reg rst,clk,cin,serial_in,direction,red_op_A,red_op_B,byPass_A,byPass_B;
reg [2:0] A,B,opcode;
wire [3:0] anode ;
wire [6:0] cathode;
wire [15:0] leds;
//wire valid;
initial begin
    clk = 0;
    forever #1 clk = ~clk;
end
integer i ;
initial begin
    rst = 1;
    cin = 0;
    serial_in = 0;
    direction = 1;// for left
    red_op_B = 0;
    red_op_A = 0;
    byPass_A = 0;
    byPass_B = 0;
    A = 'b001;
    B = 'b010;
    opcode = 000; // for AND operation
    #2;
    // for checking bypass A
    byPass_A = 1;
    //byPass_B = 0;
    rst = 0;

```

```

#4;
// for checking bypass B
byPass_A = 0;
byPass_B = 1;
#2;
//for checking input priority
A = 'b111;
B = 'b100;
#4;
byPass_A = 1;
#2;
byPass_A = 0;
byPass_B = 0;
rst = 1;
#2;
//then go through opcode case
rst = 0;
//#2;
// for reduction A
red_op_A = 1;
red_op_B = 0;
#2;
//for reduction B
red_op_A = 0;
red_op_B = 1;
#2;
// checking input priority to reduction operation opcode = 000 (AND)
red_op_A = 1;
#2;
// bitwise AND --> out = A & B
red_op_A = 0;
red_op_B = 0;
#2;
// the same operation at opcode = 001 XOR(^) so i'll write only one case
// bit wise XOR
opcode = 'b001;
#2;
//addition
A = 'b010;
B = 'b011;
opcode = 'b010;
#2;
opcode = 'b011;//multiplication
#2;
// check invalid case when not logic opcode but use red-op-a

```


```

red_op_A = 1;
#20;// blinking working well
rst = 1;
red_op_A = 0;
red_op_B = 0;
#2;
rst = 0;
opcode = 'b100;// left operation for each clk posedge then put long delay and
random for serial_in
for(i = 0;i<10;i = i+1) begin
    @(negedge clk)
    serial_in = $random;
end
#2;
direction = 0;
for(i = 0;i<10;i = i+1) begin
    @(negedge clk)
    serial_in = $random;
end
#2;
opcode = 'b101;
#2;
direction = 1;
#10;
direction = 0;
#10;
$stop;
end
ALSU_TO_SEVEN_SEGMENT
DUT(A,B,opcode,cin,serial_in,direction,red_op_A,red_op_B,byPass_A,byPass_B,clk,rst,anode,cathode,leds);
endmodule


```

2)Snippets:

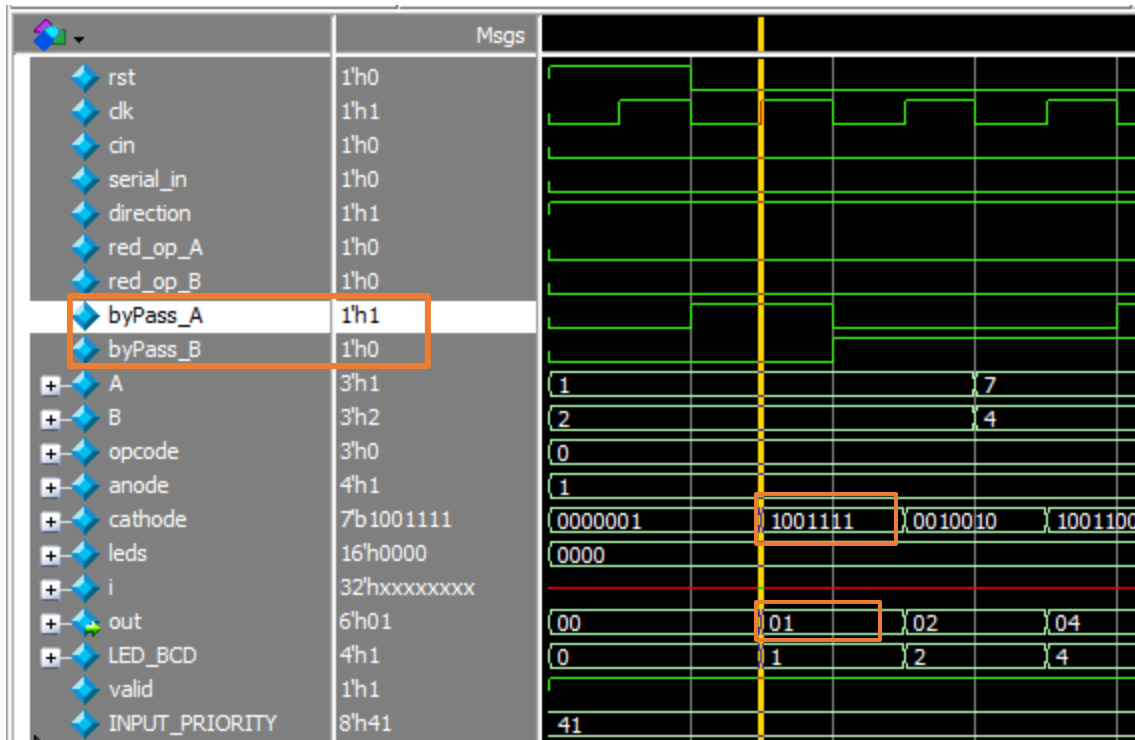
1. At start reset is high for 2 time unit as delay so output is 0,then deactivated reset and now bypass A is high so out is equal to A which is shown in the following figure also Cathode is activated by B , C led only to display one.



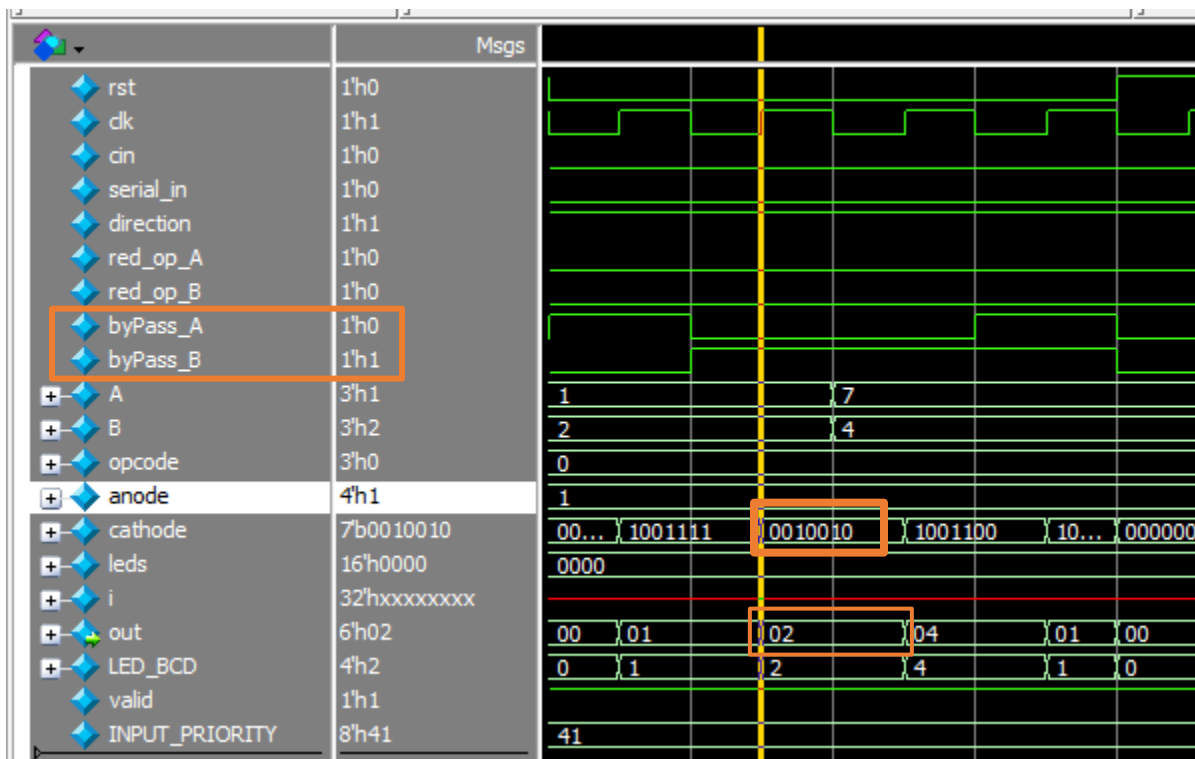
2. Here ByPass B is active then out = B which is 2 and cathode is activated by abdeg leds to display 2.



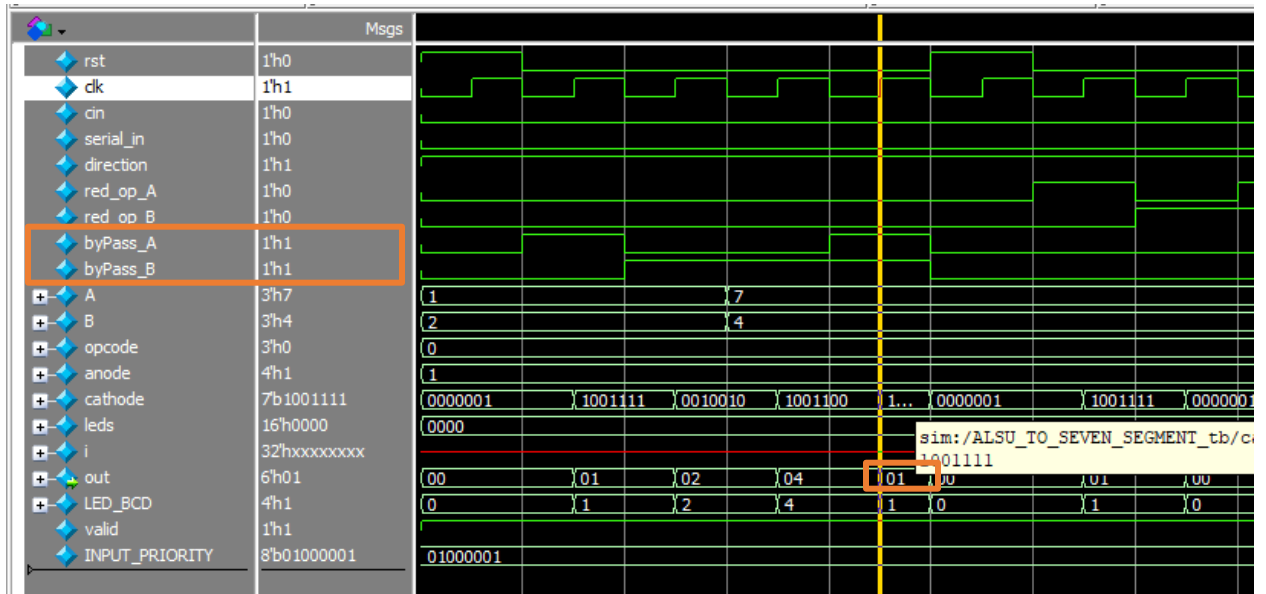
3. Here both bypass a,b are high then take the value of INPUTPRIORITY parameter only least six bits which is one.




4. Reduction operation for A.

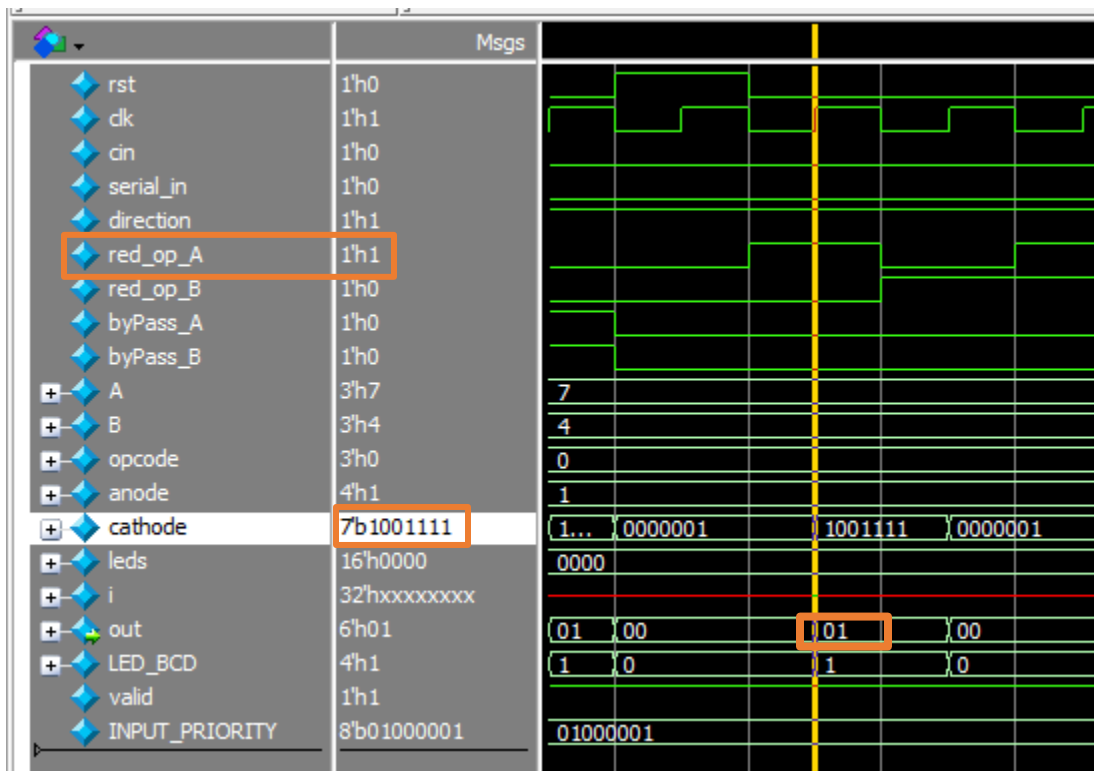

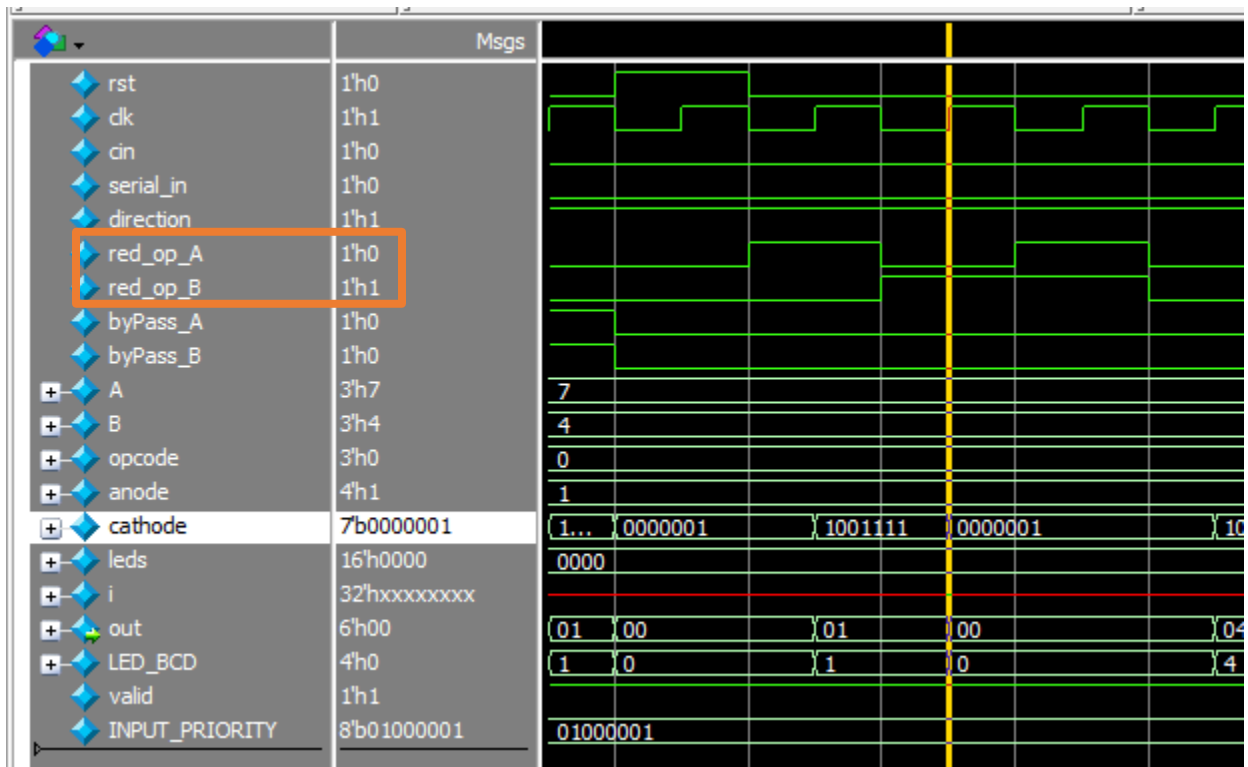
5. Reduction operation for B [4 in decimal]



 
6. And operation between A (7) & B (4) = 4



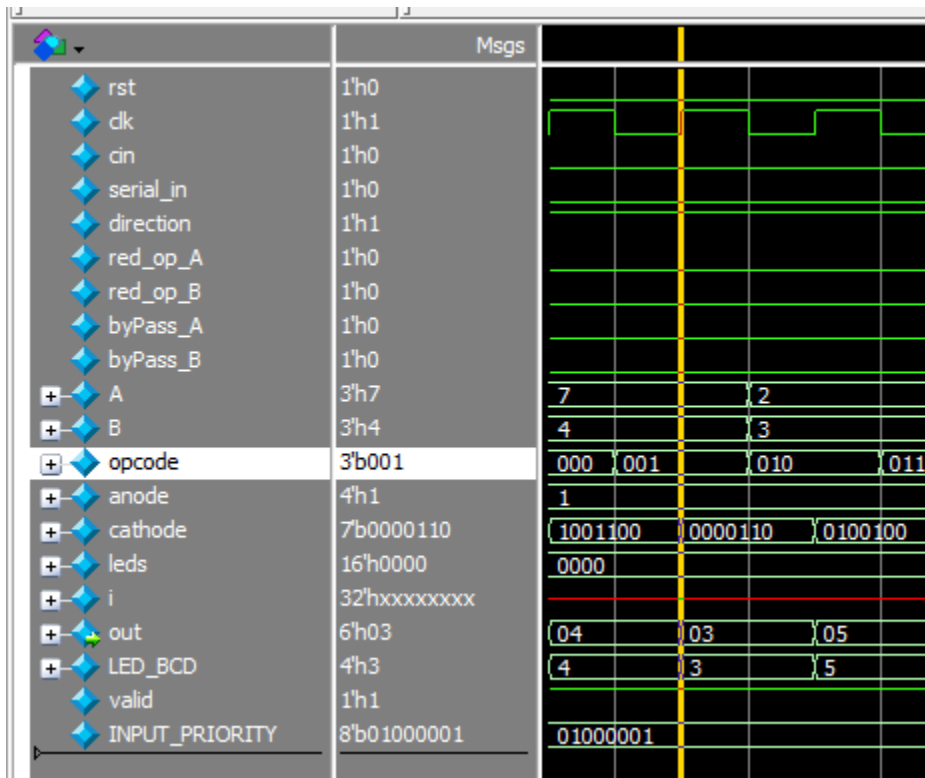
7. Opcode = 001 Xor operation between $A \wedge B$




8. Addition and multiplication for A , B

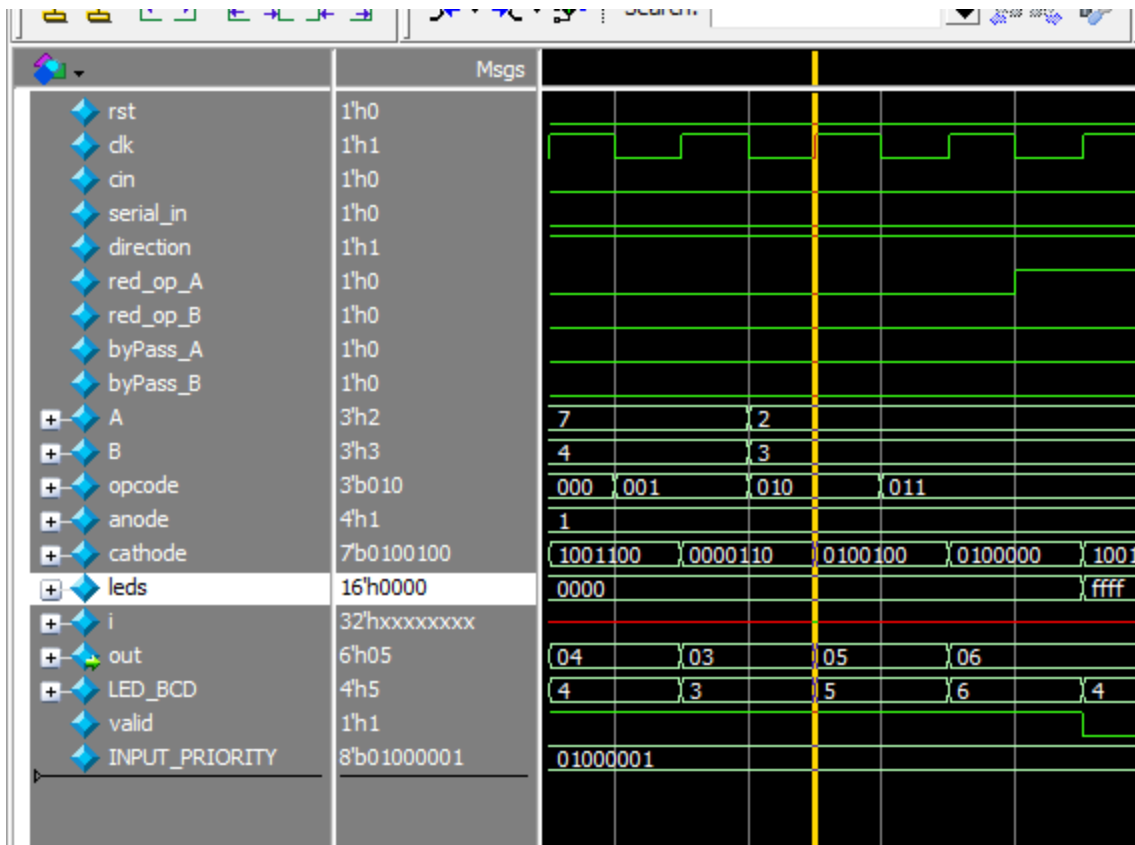

 
**9. Invalid case opcode not logic op but red_op_A is high
Then leds are blinking**



 
10. Shift operation before vertical yellow line is left shift and after that is shift right





 
11. Finally with opcode 101 there is rotate operation where direction is high then rotate to left otherwise rotate to the right



3) Synthesis :

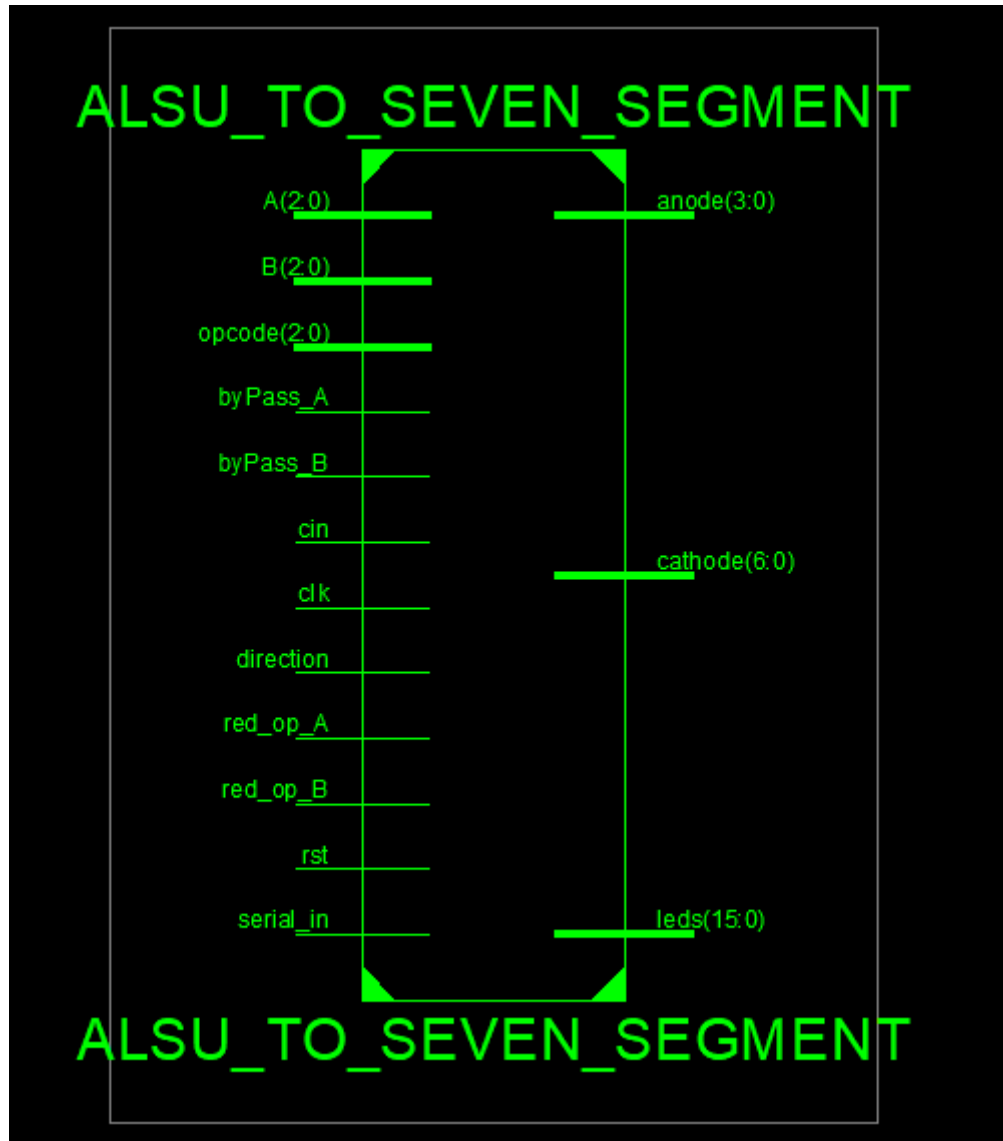

 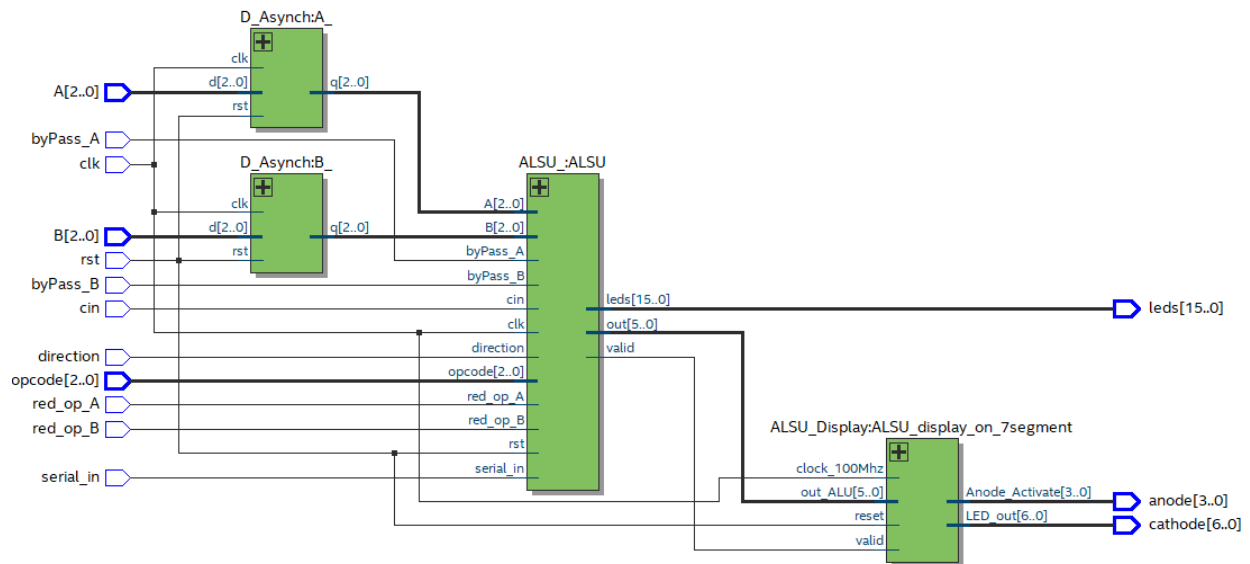

 

4)XDC :

```
## This file is a general .xdc for the Basys3 rev B board
## To use it in a project:
## - uncomment the lines corresponding to used pins
## - rename the used ports (in each line, after get_ports) according to the top
level signal names in the project
## Clock signal
```

```

set_property -dict { PACKAGE_PIN W5      IOSTANDARD LVCMOS33 } [get_ports clk]
#create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports
clk]

## Switches
set_property -dict { PACKAGE_PIN V17      IOSTANDARD LVCMOS33 } [get_ports
opcode[0]]
set_property -dict { PACKAGE_PIN V16      IOSTANDARD LVCMOS33 } [get_ports
opcode[1]]
set_property -dict { PACKAGE_PIN W16      IOSTANDARD LVCMOS33 } [get_ports
opcode[2]]
set_property -dict { PACKAGE_PIN W17      IOSTANDARD LVCMOS33 } [get_ports A[0]]
set_property -dict { PACKAGE_PIN W15      IOSTANDARD LVCMOS33 } [get_ports A[1]]
set_property -dict { PACKAGE_PIN V15      IOSTANDARD LVCMOS33 } [get_ports A[2]]
set_property -dict { PACKAGE_PIN W14      IOSTANDARD LVCMOS33 } [get_ports B[0]]
set_property -dict { PACKAGE_PIN W13      IOSTANDARD LVCMOS33 } [get_ports B[1]]
set_property -dict { PACKAGE_PIN V2       IOSTANDARD LVCMOS33 } [get_ports B[2]]
set_property -dict { PACKAGE_PIN T3       IOSTANDARD LVCMOS33 } [get_ports cin]
set_property -dict { PACKAGE_PIN T2       IOSTANDARD LVCMOS33 } [get_ports red_op_A]
set_property -dict { PACKAGE_PIN R3       IOSTANDARD LVCMOS33 } [get_ports red_op_B]
set_property -dict { PACKAGE_PIN W2       IOSTANDARD LVCMOS33 } [get_ports byPass_A]
set_property -dict { PACKAGE_PIN U1       IOSTANDARD LVCMOS33 } [get_ports byPass_B]
set_property -dict { PACKAGE_PIN T1       IOSTANDARD LVCMOS33 } [get_ports
direction]
set_property -dict { PACKAGE_PIN R2       IOSTANDARD LVCMOS33 } [get_ports
serial_in]

## LEDs
set_property -dict { PACKAGE_PIN U16      IOSTANDARD LVCMOS33 } [get_ports leds[0]]
set_property -dict { PACKAGE_PIN E19      IOSTANDARD LVCMOS33 } [get_ports leds[1]]
set_property -dict { PACKAGE_PIN U19      IOSTANDARD LVCMOS33 } [get_ports leds[2]]
set_property -dict { PACKAGE_PIN V19      IOSTANDARD LVCMOS33 } [get_ports leds[3]]
set_property -dict { PACKAGE_PIN W18      IOSTANDARD LVCMOS33 } [get_ports leds[4]]
set_property -dict { PACKAGE_PIN U15      IOSTANDARD LVCMOS33 } [get_ports leds[5]]
set_property -dict { PACKAGE_PIN U14      IOSTANDARD LVCMOS33 } [get_ports leds[6]]
set_property -dict { PACKAGE_PIN V14      IOSTANDARD LVCMOS33 } [get_ports leds[7]]
set_property -dict { PACKAGE_PIN V13      IOSTANDARD LVCMOS33 } [get_ports leds[8]]
set_property -dict { PACKAGE_PIN V3       IOSTANDARD LVCMOS33 } [get_ports leds[9]]
set_property -dict { PACKAGE_PIN W3       IOSTANDARD LVCMOS33 } [get_ports leds[10]]
set_property -dict { PACKAGE_PIN U3       IOSTANDARD LVCMOS33 } [get_ports leds[11]]
set_property -dict { PACKAGE_PIN P3       IOSTANDARD LVCMOS33 } [get_ports leds[12]]
set_property -dict { PACKAGE_PIN N3       IOSTANDARD LVCMOS33 } [get_ports leds[13]]
set_property -dict { PACKAGE_PIN P1       IOSTANDARD LVCMOS33 } [get_ports leds[14]]

```

```

set_property -dict { PACKAGE_PIN L1      IOSTANDARD LVCMOS33 } [get_ports leds[15]]

##7 Segment Display
set_property -dict { PACKAGE_PIN W7      IOSTANDARD LVCMOS33 } [get_ports
cathode[6]]
set_property -dict { PACKAGE_PIN W6      IOSTANDARD LVCMOS33 } [get_ports
cathode[5]]
set_property -dict { PACKAGE_PIN U8      IOSTANDARD LVCMOS33 } [get_ports
cathode[4]]
set_property -dict { PACKAGE_PIN V8      IOSTANDARD LVCMOS33 } [get_ports
cathode[3]]
set_property -dict { PACKAGE_PIN U5      IOSTANDARD LVCMOS33 } [get_ports
cathode[2]]
set_property -dict { PACKAGE_PIN V5      IOSTANDARD LVCMOS33 } [get_ports
cathode[1]]
set_property -dict { PACKAGE_PIN U7      IOSTANDARD LVCMOS33 } [get_ports
cathode[0]]

#set_property -dict { PACKAGE_PIN V7      IOSTANDARD LVCMOS33 } [get_ports dp]

set_property -dict { PACKAGE_PIN U2      IOSTANDARD LVCMOS33 } [get_ports anode[0]]
set_property -dict { PACKAGE_PIN U4      IOSTANDARD LVCMOS33 } [get_ports anode[1]]
set_property -dict { PACKAGE_PIN V4      IOSTANDARD LVCMOS33 } [get_ports anode[2]]
set_property -dict { PACKAGE_PIN W4      IOSTANDARD LVCMOS33 } [get_ports anode[3]]

##Buttons
set_property -dict { PACKAGE_PIN U18      IOSTANDARD LVCMOS33 } [get_ports rst]
#set_property -dict { PACKAGE_PIN T18      IOSTANDARD LVCMOS33 } [get_ports btnU]
#set_property -dict { PACKAGE_PIN W19      IOSTANDARD LVCMOS33 } [get_ports btnL]
#set_property -dict { PACKAGE_PIN T17      IOSTANDARD LVCMOS33 } [get_ports btnR]
#set_property -dict { PACKAGE_PIN U17      IOSTANDARD LVCMOS33 } [get_ports btnD]

##Pmod Header JA
#set_property -dict { PACKAGE_PIN J1      IOSTANDARD LVCMOS33 } [get_ports
{JA[0]}};#Sch name = JA1
#set_property -dict { PACKAGE_PIN L2      IOSTANDARD LVCMOS33 } [get_ports
{JA[1]}};#Sch name = JA2
#set_property -dict { PACKAGE_PIN J2      IOSTANDARD LVCMOS33 } [get_ports
{JA[2]}};#Sch name = JA3
#set_property -dict { PACKAGE_PIN G2      IOSTANDARD LVCMOS33 } [get_ports
{JA[3]}};#Sch name = JA4

```

```

#set_property -dict { PACKAGE_PIN H1    IOSTANDARD LVCMOS33 } [get_ports
{JA[4]}};#Sch name = JA7
#set_property -dict { PACKAGE_PIN K2    IOSTANDARD LVCMOS33 } [get_ports
{JA[5]}};#Sch name = JA8
#set_property -dict { PACKAGE_PIN H2    IOSTANDARD LVCMOS33 } [get_ports
{JA[6]}};#Sch name = JA9
#set_property -dict { PACKAGE_PIN G3    IOSTANDARD LVCMOS33 } [get_ports
{JA[7]}};#Sch name = JA10

##Pmod Header JB
#set_property -dict { PACKAGE_PIN A14    IOSTANDARD LVCMOS33 } [get_ports
{JB[0]}};#Sch name = JB1
#set_property -dict { PACKAGE_PIN A16    IOSTANDARD LVCMOS33 } [get_ports
{JB[1]}};#Sch name = JB2
#set_property -dict { PACKAGE_PIN B15    IOSTANDARD LVCMOS33 } [get_ports
{JB[2]}};#Sch name = JB3
#set_property -dict { PACKAGE_PIN B16    IOSTANDARD LVCMOS33 } [get_ports
{JB[3]}};#Sch name = JB4
#set_property -dict { PACKAGE_PIN A15    IOSTANDARD LVCMOS33 } [get_ports
{JB[4]}};#Sch name = JB7
#set_property -dict { PACKAGE_PIN A17    IOSTANDARD LVCMOS33 } [get_ports
{JB[5]}};#Sch name = JB8
#set_property -dict { PACKAGE_PIN C15    IOSTANDARD LVCMOS33 } [get_ports
{JB[6]}};#Sch name = JB9
#set_property -dict { PACKAGE_PIN C16    IOSTANDARD LVCMOS33 } [get_ports
{JB[7]}};#Sch name = JB10

##Pmod Header JC
#set_property -dict { PACKAGE_PIN K17    IOSTANDARD LVCMOS33 } [get_ports
{JC[0]}};#Sch name = JC1
#set_property -dict { PACKAGE_PIN M18    IOSTANDARD LVCMOS33 } [get_ports
{JC[1]}};#Sch name = JC2
#set_property -dict { PACKAGE_PIN N17    IOSTANDARD LVCMOS33 } [get_ports
{JC[2]}};#Sch name = JC3
#set_property -dict { PACKAGE_PIN P18    IOSTANDARD LVCMOS33 } [get_ports
{JC[3]}};#Sch name = JC4
#set_property -dict { PACKAGE_PIN L17    IOSTANDARD LVCMOS33 } [get_ports
{JC[4]}};#Sch name = JC7
#set_property -dict { PACKAGE_PIN M19    IOSTANDARD LVCMOS33 } [get_ports
{JC[5]}};#Sch name = JC8
#set_property -dict { PACKAGE_PIN P17    IOSTANDARD LVCMOS33 } [get_ports
{JC[6]}};#Sch name = JC9
#set_property -dict { PACKAGE_PIN R18    IOSTANDARD LVCMOS33 } [get_ports
{JC[7]}};#Sch name = JC10

```

```

##Pmod Header JXADC
#set_property -dict { PACKAGE_PIN J3      IOSTANDARD LVCMOS33 } [get_ports
{JXADC[0]}};#Sch name = XA1_P
#set_property -dict { PACKAGE_PIN L3      IOSTANDARD LVCMOS33 } [get_ports
{JXADC[1]}};#Sch name = XA2_P
#set_property -dict { PACKAGE_PIN M2      IOSTANDARD LVCMOS33 } [get_ports
{JXADC[2]}};#Sch name = XA3_P
#set_property -dict { PACKAGE_PIN N2      IOSTANDARD LVCMOS33 } [get_ports
{JXADC[3]}};#Sch name = XA4_P
#set_property -dict { PACKAGE_PIN K3      IOSTANDARD LVCMOS33 } [get_ports
{JXADC[4]}};#Sch name = XA1_N
#set_property -dict { PACKAGE_PIN M3      IOSTANDARD LVCMOS33 } [get_ports
{JXADC[5]}};#Sch name = XA2_N
#set_property -dict { PACKAGE_PIN M1      IOSTANDARD LVCMOS33 } [get_ports
{JXADC[6]}};#Sch name = XA3_N
#set_property -dict { PACKAGE_PIN N1      IOSTANDARD LVCMOS33 } [get_ports
{JXADC[7]}};#Sch name = XA4_N

##VGA Connector
#set_property -dict { PACKAGE_PIN G19      IOSTANDARD LVCMOS33 } [get_ports
{vgaRed[0]}}
#set_property -dict { PACKAGE_PIN H19      IOSTANDARD LVCMOS33 } [get_ports
{vgaRed[1]}}
#set_property -dict { PACKAGE_PIN J19      IOSTANDARD LVCMOS33 } [get_ports
{vgaRed[2]}}
#set_property -dict { PACKAGE_PIN N19      IOSTANDARD LVCMOS33 } [get_ports
{vgaRed[3]}}
#set_property -dict { PACKAGE_PIN N18      IOSTANDARD LVCMOS33 } [get_ports
{vgaBlue[0]}}
#set_property -dict { PACKAGE_PIN L18      IOSTANDARD LVCMOS33 } [get_ports
{vgaBlue[1]}}
#set_property -dict { PACKAGE_PIN K18      IOSTANDARD LVCMOS33 } [get_ports
{vgaBlue[2]}}
#set_property -dict { PACKAGE_PIN J18      IOSTANDARD LVCMOS33 } [get_ports
{vgaBlue[3]}}
#set_property -dict { PACKAGE_PIN J17      IOSTANDARD LVCMOS33 } [get_ports
{vgaGreen[0]}}
#set_property -dict { PACKAGE_PIN H17      IOSTANDARD LVCMOS33 } [get_ports
{vgaGreen[1]}}
#set_property -dict { PACKAGE_PIN G17      IOSTANDARD LVCMOS33 } [get_ports
{vgaGreen[2]}}
#set_property -dict { PACKAGE_PIN D17      IOSTANDARD LVCMOS33 } [get_ports
{vgaGreen[3]}}
#set_property -dict { PACKAGE_PIN P19      IOSTANDARD LVCMOS33 } [get_ports Hsync]

```



```

#set_property -dict { PACKAGE_PIN R19      IOSTANDARD LVCMOS33 } [get_ports Vsync]

##USB-RS232 Interface
#set_property -dict { PACKAGE_PIN B18      IOSTANDARD LVCMOS33 } [get_ports RsRx]
#set_property -dict { PACKAGE_PIN A18      IOSTANDARD LVCMOS33 } [get_ports RsTx]

##USB HID (PS/2)
#set_property -dict { PACKAGE_PIN C17      IOSTANDARD LVCMOS33      PULLUP true }
[get_ports PS2Clk]
#set_property -dict { PACKAGE_PIN B17      IOSTANDARD LVCMOS33      PULLUP true }
[get_ports PS2Data]

##Quad SPI Flash
##Note that CCLK_0 cannot be placed in 7 series devices. You can access it using
the
##STARTUPE2 primitive.
#set_property -dict { PACKAGE_PIN D18      IOSTANDARD LVCMOS33 } [get_ports
{QspiDB[0]}]
#set_property -dict { PACKAGE_PIN D19      IOSTANDARD LVCMOS33 } [get_ports
{QspiDB[1]}]
#set_property -dict { PACKAGE_PIN G18      IOSTANDARD LVCMOS33 } [get_ports
{QspiDB[2]}]
#set_property -dict { PACKAGE_PIN F18      IOSTANDARD LVCMOS33 } [get_ports
{QspiDB[3]}]
#set_property -dict { PACKAGE_PIN K19      IOSTANDARD LVCMOS33 } [get_ports QspiCSn]

## Configuration options, can be used for all designs
set_property CONFIG_VOLTAGE 3.3 [current_design]
set_property CFGBVS VCC0 [current_design]

## SPI configuration mode options for QSPI boot, can be used for all designs
set_property BITSTREAM.GENERAL.COMPRESS TRUE [current_design]
set_property BITSTREAM.CONFIG.CONFIGRATE 33 [current_design]
set_property CONFIG_MODE SPIx4 [current_design]

```

5)Sources Files:

<https://drive.google.com/drive/folders/1yqP9wNd3dxJazNdYnQVOibtIw5X8h21X?usp=sharing>

Thanks